

中山大学数据科学与计算机学院本科生实验报告

(2019 学年秋季学期)

课程名称：计算机组成原理实验

任课教师：郭雪梅

助教：汪庭葳、刘洋旗

年级&班级	2018 级计科一班	专业(方向)	计算机类
学号	18340013	姓名	陈琮昊
电话	15734867907	Email	1062080021@qq.com
开始日期	2019. 10. 23	完成日期	2019. 11. 5

一、实验题目：VIVADO 实验一

二、实验目的：用 VIVADO 实现加减法器

三、实验内容

1. 实验步骤：


(i) 实现 4 位超前进位加法器设计并仿真实现

(ii) 设计 8 位的加减法器

2. 实验原理：加法器的原理

四、实验结果：


(I) 4 位超前进位加法器仿真结果：

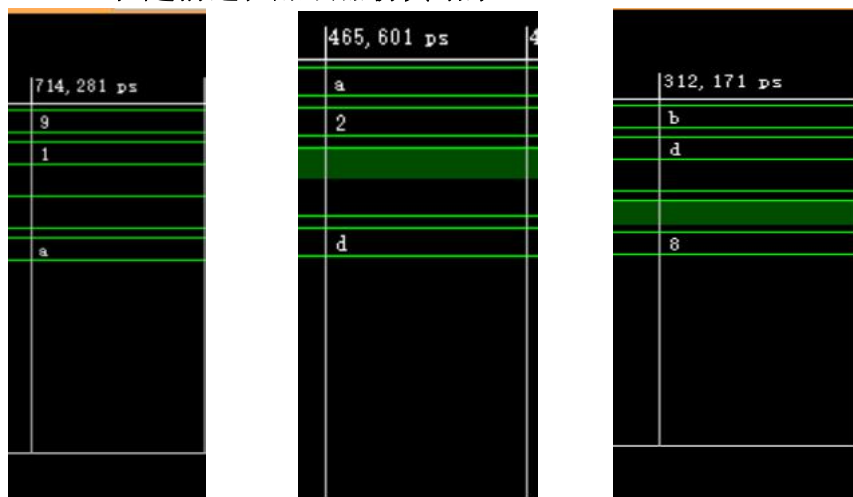

如图：9+1+0=0a a+2+1=0d b+d+0=18（均为 16 进制，第三行为进位）


(II) 8 位的加减法器结果:

1.Run Simulation:

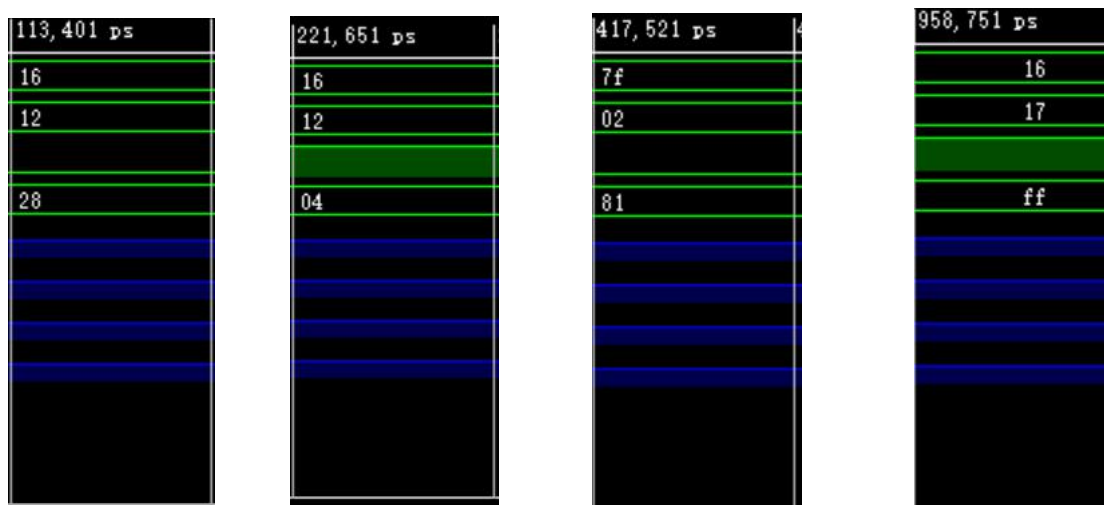



如图: $16+12=28$, $16-12=04$, $7f+02=81$, $16-17=ff$ (16 进制, 第三行 0 加 1 减)。

2. RTL Analysis:

 

3. Run Implementation&&Generate Bitstream

4. 烧 FPGA 板, 结果如下:

  

如图所示：最左面 8 位为第二个数的从低到高位，右面 8 位为第一个数的从低到高位。第一张为减法（ $20-34=-14=-128+64+32+16+2$ ），第二张为加法（ $20+34=54=32+16+4+2$ ），核对可知结果正确，实验成功。

五、实验感想：本次实验主要是用 VIVADO 设计加减法器，其中超前进位的实验只需要仿真，比较简单；重点在于第二个实验：8 位的加减法器，该实验是按照完整的流程来的。第一次使用 VIVADO 遇到了许多状况，比如需要 valid license，在网上找到 license 后可以正常使用 VIVADO 了；解决该问题后遇到的又一个瓶颈是烧板，该过程有时会不稳定，需要耐心；还有个小问题就是连接引脚，这倒不是很难解决的问题，但真的需要特别细心，才能保证不出错并且顺利连接板，从而显示正确的结果。不过最后看到板上显示正确结果的时候还是很开心的。

附录（流程图，注释过的代码）：

（1）4 位超前进位加法器代码：

```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

module chaoadder(A,B,C0,C4,F);
    input[3:0] A,B;
    input      C0;
    output[3:0] F;
    output      C4;
    wire[3:0]    A,B;
    reg [3:0]    F,G,P;
    reg          C4;
    reg  C1,C2,C3;
    always@(*)
    begin
        G[0]=A[0]&B[0];
        G[1]=A[1]&B[1];
        G[2]=A[2]&B[2];
        G[3]=A[3]&B[3];

        P[0]=A[0]|B[0];
        P[1]=A[1]|B[1];
        P[2]=A[2]|B[2];
        P[3]=A[3]|B[3];

        C1=G[0]|(P[0]&C0);
        C2=G[1]|(P[1]&C1);
        C3=G[2]|(P[2]&C2);
        C4=G[3]|(P[3]&C3);

        F[0]=A[0]^B[0]^C0;
        F[1]=A[1]^B[1]^C1;
        F[2]=A[2]^B[2]^C2;
```

```
F[3]=A[3]^B[3]^C3;
```

```
end
```

```
endmodule
```

仿真实现:

```
`timescale 1ns / 1ps
```

```
module simadder(
```

```
);
```

```
// Inputs
```

```
    reg [3:0] A;
```

```
    reg [3:0] B;
```

```
    reg C0;
```

```
// Outputs
```

```
    wire C4;
```

```
    wire [3:0] F;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
    chaoadder uut
```

```
        (.A(A),
```

```
        .B(B),
```

```
        .C0(C0),
```

```
        .C4(C4),
```

```
        .F(F)
```

```
    );
```

```
initial begin
```

```
    // Initialize Inputs
```

```
        C0 = 0;
```

```
    // Wait 100 ns for global reset to finish
```

```
        #100;
```

```
// Add stimulus here
```

```
    begin A = 'B1100;B='B1011;C0 = 0;end
```

```

        #100;

        begin A = 'B1011;B='B0010;C0 = 1;end

        #100;

        begin A = 'B1011;B='B1101;C0 = 0;end

        #100;

        begin A = 'B1010;B='B0010;C0 = 1;end

        #100;

        A = 'B0111;B='B1000;C0= 0;

        #100;

        begin A = 'B0011;B='B0100;C0 = 1;end

        #100;

        begin A = 'B1001;B='B0001;C0 = 0;end

        #100;

    end

endmodule

```

(2) 8 位的加减法器代码:

```

module addsub
#(parameter WIDTH=8)           //指定数据宽度参数，缺省值是8
(
    input [(WIDTH-1):0] a,      // 缺省位数由参数WIDTH决定
    input [(WIDTH-1):0] b,
    input  sub,                 // =1为减法
    output [(WIDTH-1):0] sum,
    output cf,                  // 进位标志
    output ovf,                 // 溢出标志
    output sf,                  // 符号标志
    output zf                    // 为0标志
);

    wire [(WIDTH-1):0] subb,subb1;
    wire cf2;    // 进位
    assign subb1 = b ^ {WIDTH{sub}}; // 对于减法是取反
    assign subb  = subb1 + sub;    // 对于减法是加1，sub=1（减法）sub=0（加法）

    assign {cf2,sum} = a + subb;

```

```

    assign {cf2,sum} = a + subb;

    assign sf = sum[WIDTH-1];

    assign zf = (sum == 0) ? 1 : 0 ;

    assign cf = cf2 ^ sub;

    assign ovf = (a[WIDTH-1] ^ sum[WIDTH-1]) & (subb[WIDTH-1] ^ sum[WIDTH-1]);

endmodule

```

仿真实现：

```

`timescale 1ns / 1ps

module addsub_sim(    );
    // input
    reg [7:0] a = 8'h16;
    reg [7:0] b = 8'h12;
    reg sub = 0;

    //output
    wire [7:0] sum;
    wire cf;
    wire ovf;
    wire sf;
    wire zf;

    // initial
    addsub U (a,b,sub,sum,cf,ovf,sf,zf);
    initial begin
        #200 sub = 1;
        #200 begin a = 8'h7f; b = 8'h2; sub = 0; end
        #200 begin a = 8'hff; b = 8'h2; sub = 0; end
        #200 begin a = 8'h16; b = 8'h17; sub = 1; end
        #200 begin a = 8'hfe; b = 8'hff; sub = 1; end

    end

endmodule

```

约束文件：

```

set_property IOSTANDARD LVCMOS33 [get_ports {a[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sum[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sum[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sum[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sum[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sum[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sum[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sum[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sum[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports cf]
set_property IOSTANDARD LVCMOS33 [get_ports ovf]
set_property IOSTANDARD LVCMOS33 [get_ports sf]
set_property IOSTANDARD LVCMOS33 [get_ports sub]
set_property IOSTANDARD LVCMOS33 [get_ports zf]
set_property PACKAGE_PIN V17 [get_ports {a[7]}]
set_property PACKAGE_PIN V16 [get_ports {a[6]}]
set_property PACKAGE_PIN W16 [get_ports {a[5]}]
set_property PACKAGE_PIN W17 [get_ports {a[4]}]
set_property PACKAGE_PIN W15 [get_ports {a[3]}]
set_property PACKAGE_PIN V15 [get_ports {a[2]}]
set_property PACKAGE_PIN W14 [get_ports {a[1]}]
set_property PACKAGE_PIN W13 [get_ports {a[0]}]

```